

Find $-\Delta V$ across each C

- g on each C

Known - Values for all C's


$$-\Delta V_{\text{batt}}$$

$$\text{series} \rightarrow C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$


$$\text{parallel} \rightarrow C_{\text{eq}} = C_1 + C_2$$

$$- g = C \Delta V \text{ or } \Delta V = \frac{g}{C}$$

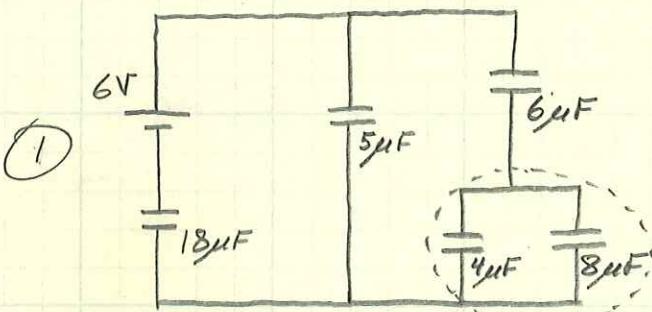
First, we need to find the equivalent capacitance of the whole circuit. I'll do it in steps, redrawing the new circuit after each step.



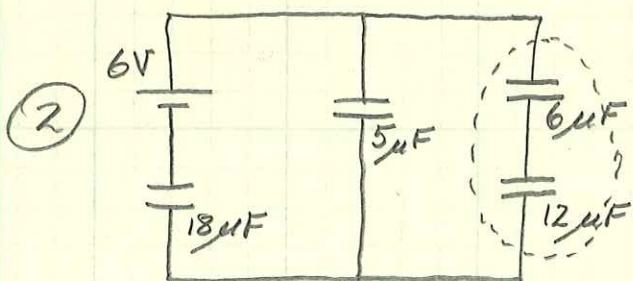
$$C_1 = 4 \mu F + 8 \mu F \\ = 12 \mu F$$


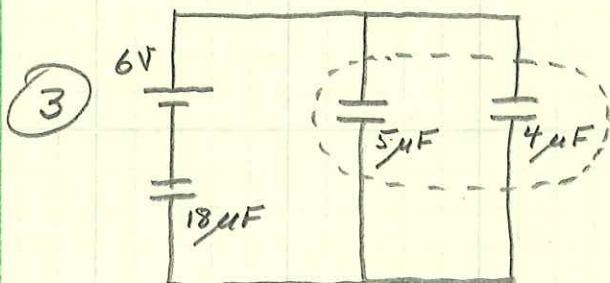
$$C_2 = \frac{(6 \mu F)(12 \mu F)}{6 \mu F + 12 \mu F} \\ = 4 \mu F$$




$$C_3 = 5 \mu F + 4 \mu F \\ = 9 \mu F$$

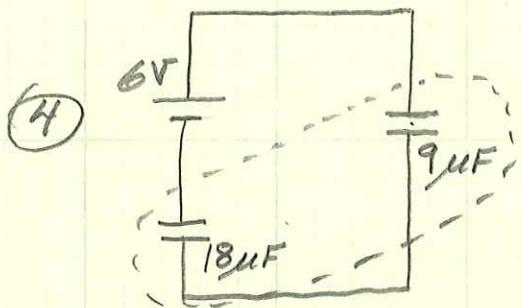

$$C_{eq} = \frac{(18\mu F)(9\mu F)}{18\mu F + 9\mu F}$$

$$= 6\mu F$$

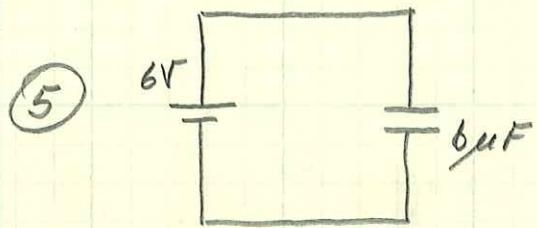

$$\Rightarrow g_{eq} = (6\mu F)(6V)$$

$$= \underline{\underline{36\mu C}}$$

Looking at circuit (4), C_{18} and C_3 are in series, so

$$g_{18} = g_3 = g_{eq}$$

$$\Rightarrow g_{18} = \underline{\underline{36\mu C}}$$

$$\Delta V_{18} = \frac{36\mu C}{18\mu F} = \underline{\underline{2V}}$$

$$(\Delta V_3 = 6V - 2V = 4V)$$

Looking at circuit (3), we now know ΔV across the $5\mu F$ capacitor (and the $4\mu F$ equivalent capacitor, C_2)

$$\Rightarrow g_5 = (5\mu F)(4V) = \underline{\underline{20\mu C}}$$

$$\Delta V_5 = \underline{\underline{4V}}$$

$$(g_2 = (4\mu F)(4V) = 16\mu C)$$

Looking at circuit ②, we now know that

$$g_2 = g_6 = g_{12}$$

$$\Rightarrow g_6 = \underline{\underline{16\mu C}}$$

$$\Delta V_6 = \frac{16\mu C}{6\mu F} = \underline{\underline{2.67V}}$$

$$(\Delta V_{12} = 4V - 2.67V = 1.33V)$$

Finally, looking at circuit ①, we know the ΔV across the $4\mu F$ and $8\mu F$ capacitors

$$\Rightarrow g_4 = (4\mu F)(1.33V) = \underline{\underline{5.33\mu C}}$$

$$\Delta V_4 = \underline{\underline{1.33V}}$$

$$g_8 = (8\mu F)(1.33V) = \underline{\underline{10.67\mu C}}$$

$$\Delta V_8 = \underline{\underline{1.33V}}$$

Summarizing

$$\Delta V_{batt} = 6.0V \quad g_{eq} = 36.0\mu C$$

$$\Delta V_{18} = 2.0V \quad g_{18} = 36.0\mu C$$

$$\Delta V_5 = 4.0V \quad g_5 = 20.0\mu C$$

$$\Delta V_6 = 2.7V \quad g_6 = 16.0\mu C$$

$$\Delta V_4 = 1.3V \quad g_4 = 5.3\mu C$$

$$\Delta V_8 = 1.3V \quad g_8 = 10.7\mu C$$