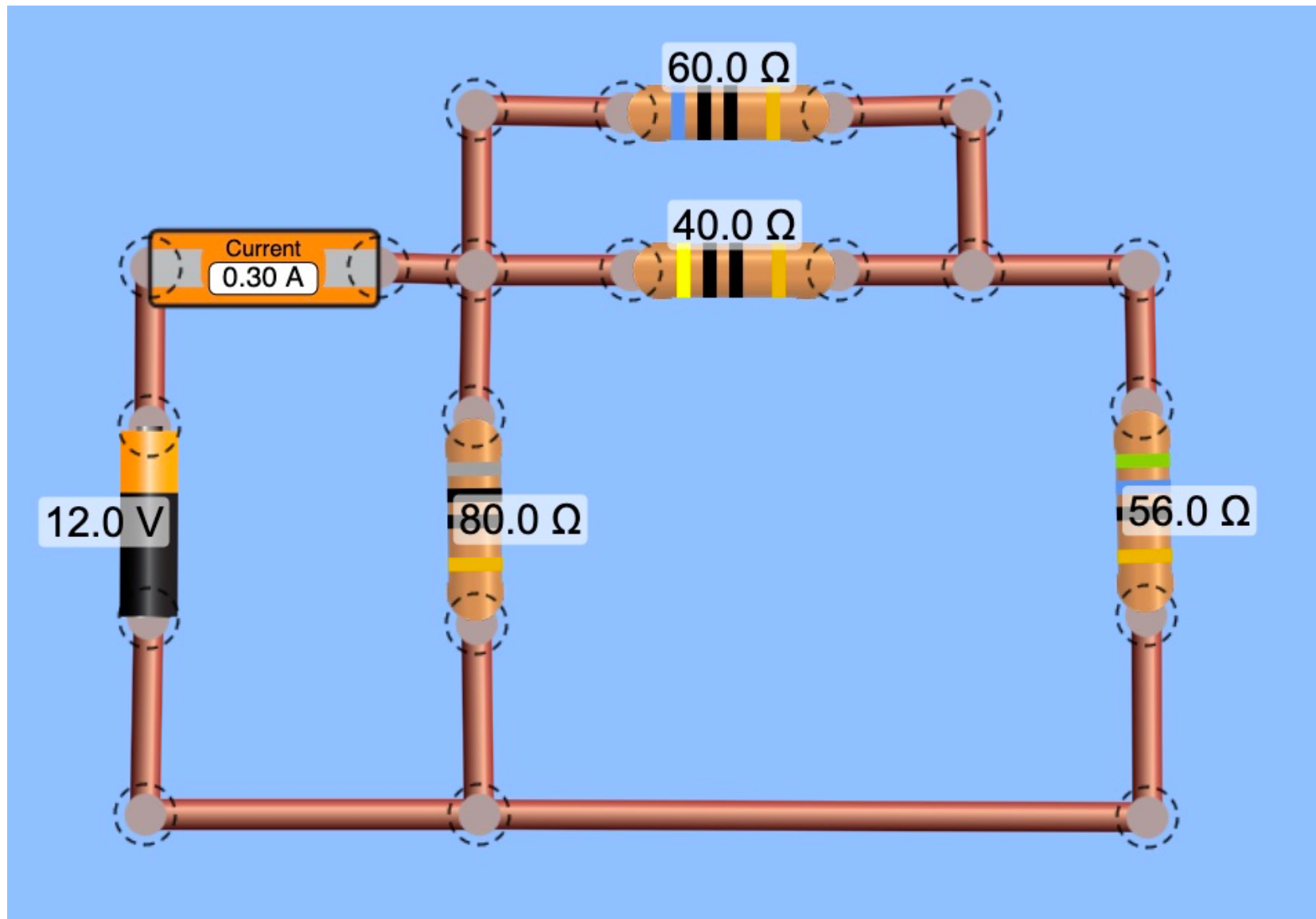



## Unit 23 – Session 3


We found in session 2 how to take resistors in series and parallel combinations and find an equivalent resistance.


Series:  $R_{eq} = R_1 + R_2 + R_3 + \dots$  (greater than largest  $R_n$ )

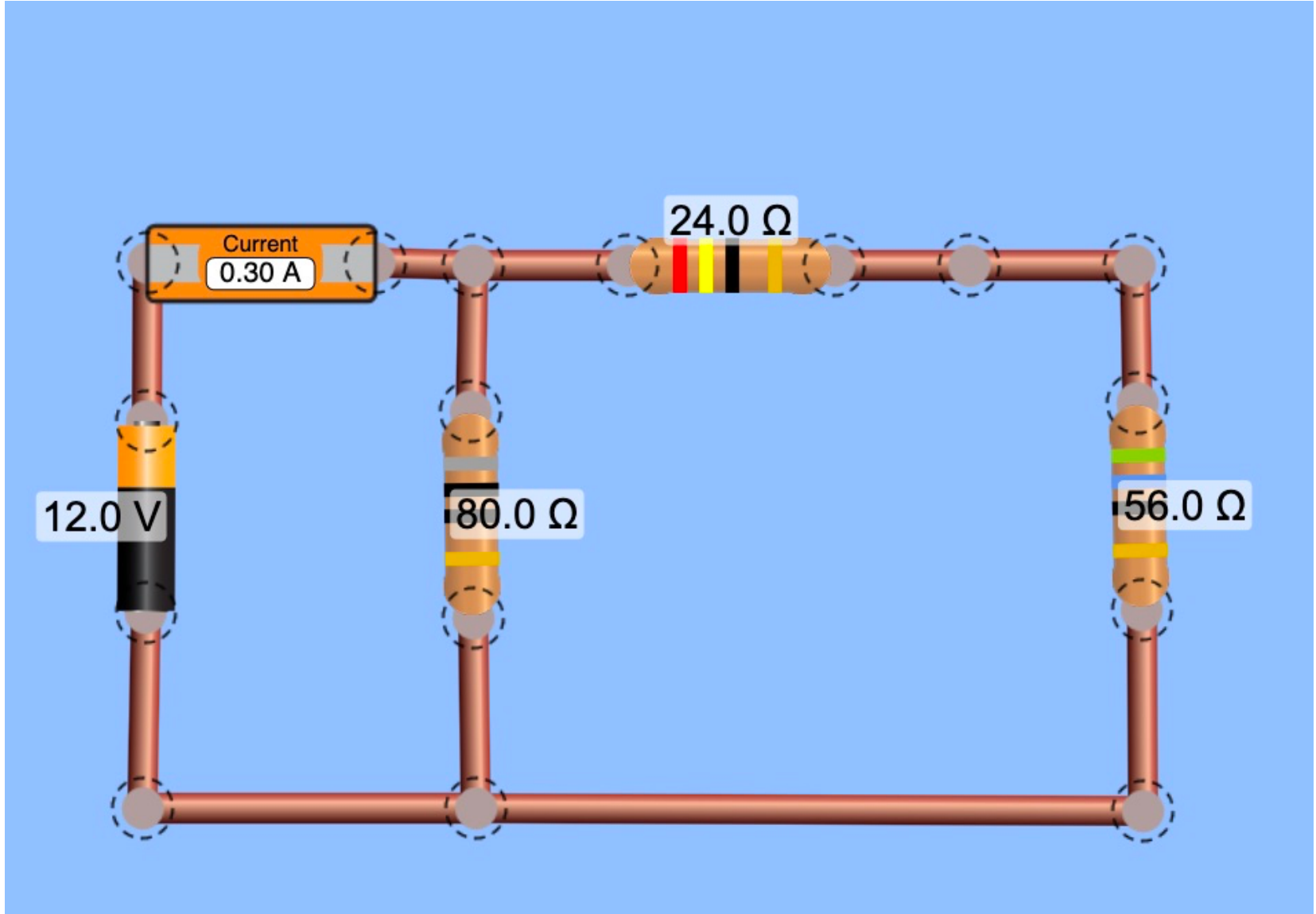Parallel:  $R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \right)^{-1}$  (less than smallest  $R_n$ )





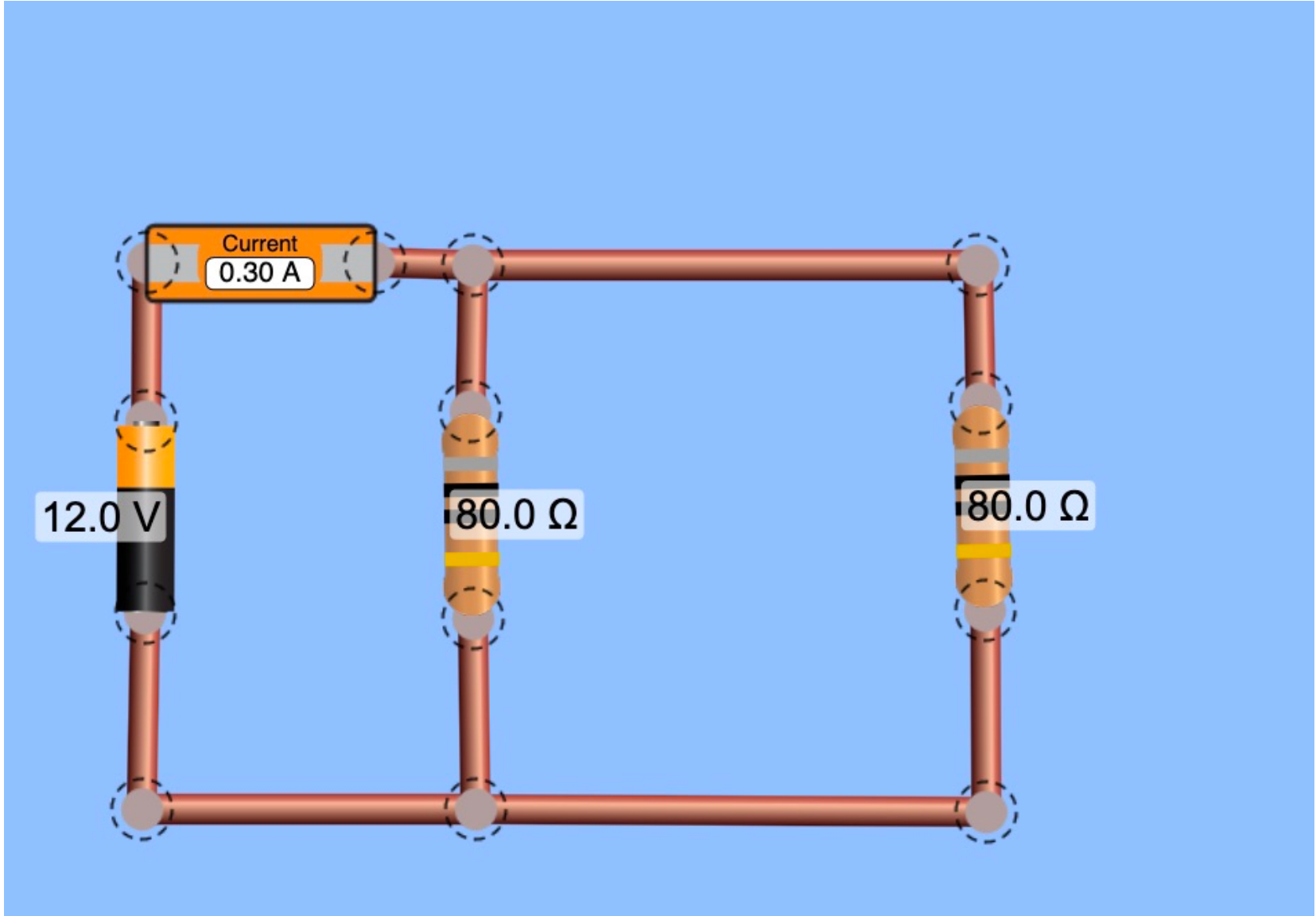

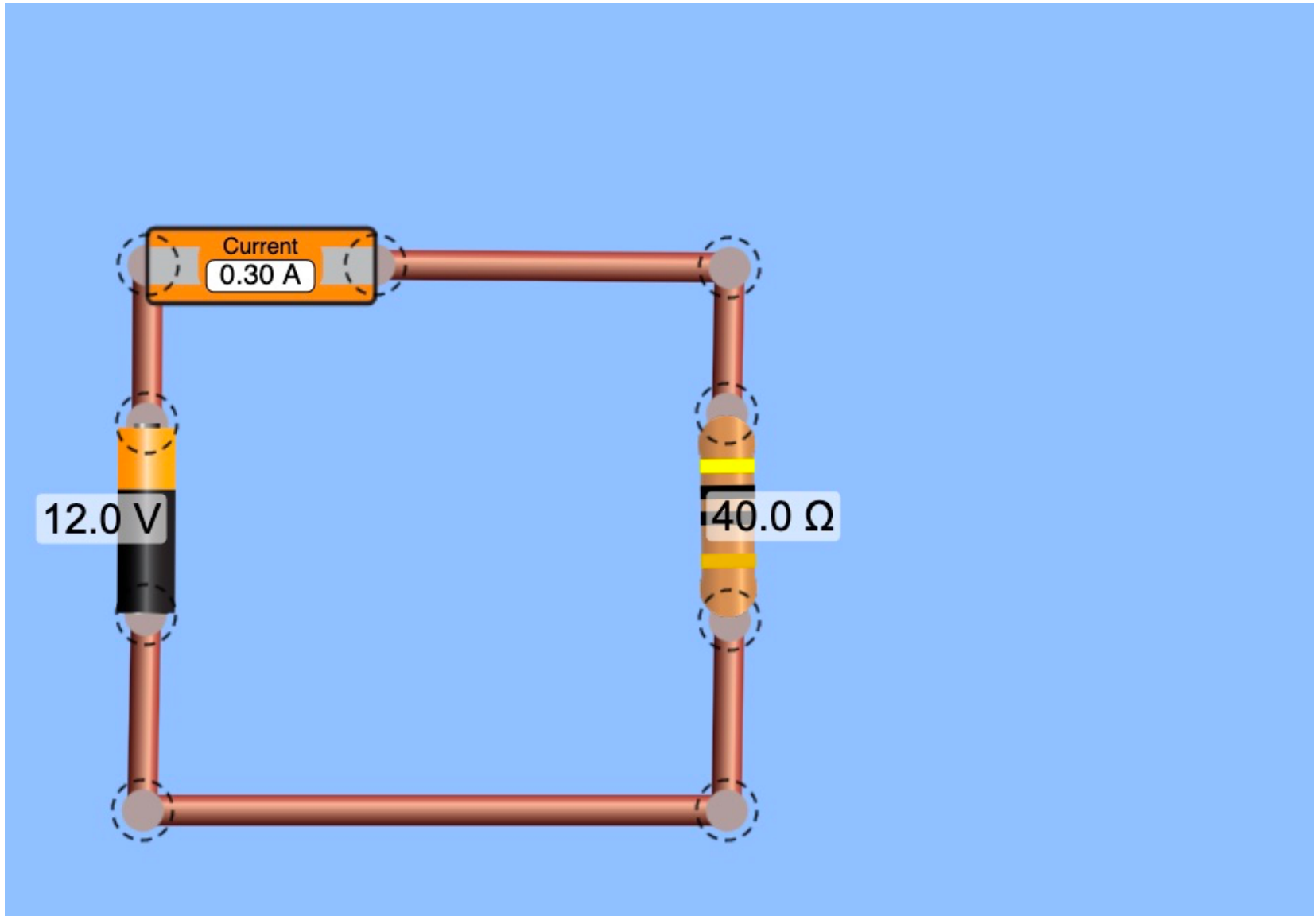


## Unit 23 – Session 3 (cont.)


Today, we are going to develop a set of laws – Kirchhoff's Laws – that will allow us to analyze these more complex circuits. The laws are very powerful, and can even be used as an alternative method to analyze parallel/series circuits that we could easily simplify.

The laws are based on two conservation laws:


- Conservation of charge.
- Conservation of energy.


Potential

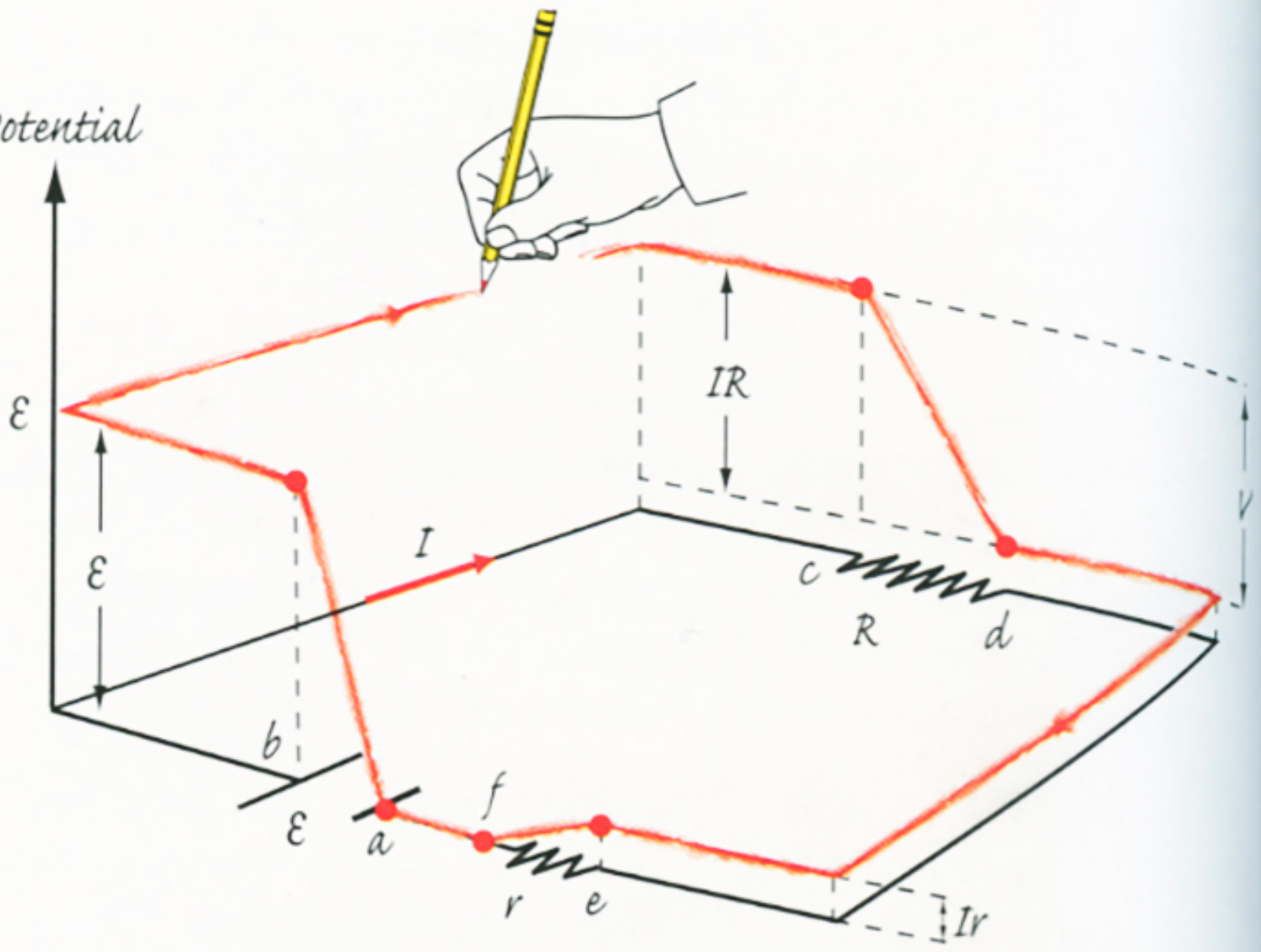


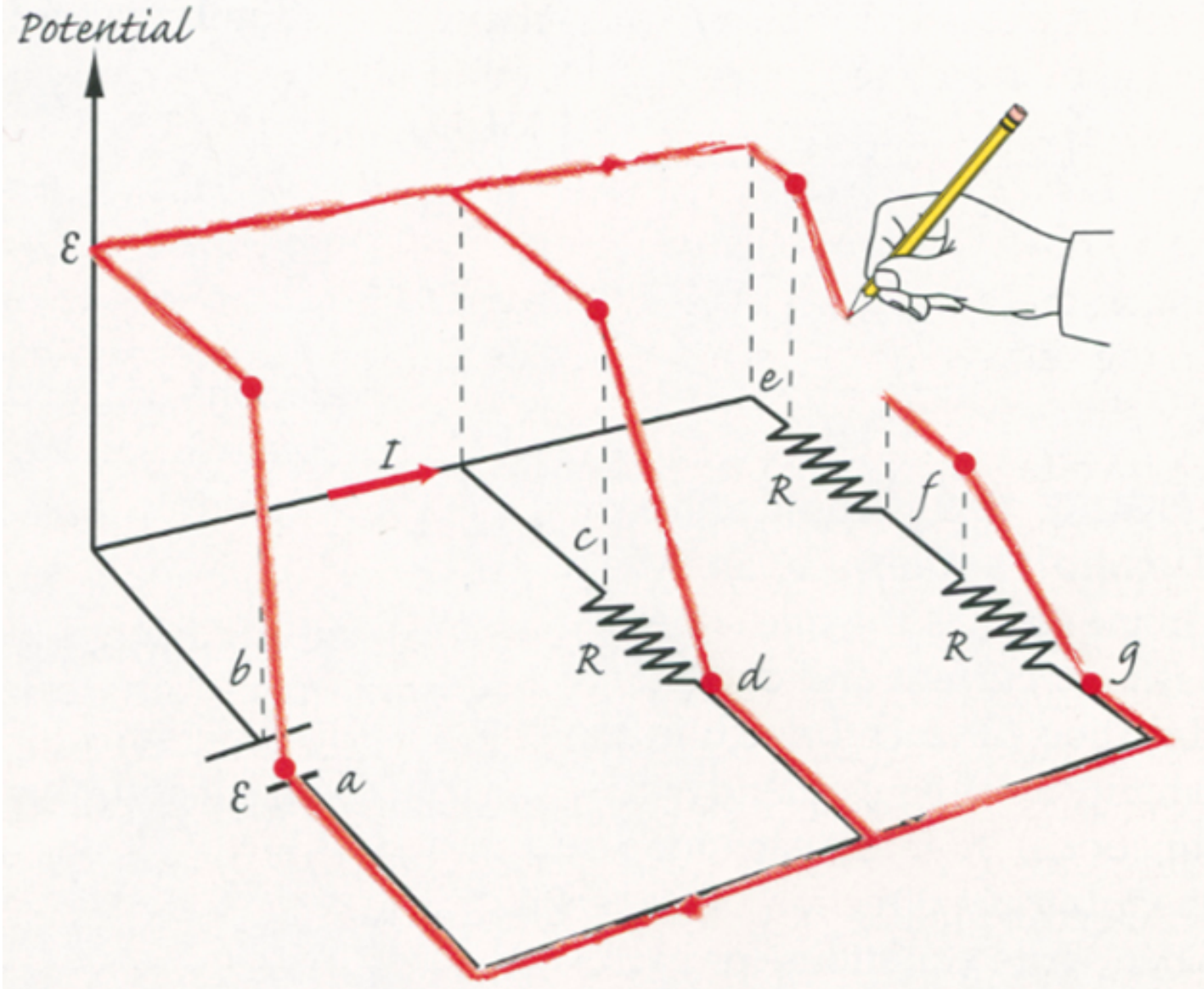




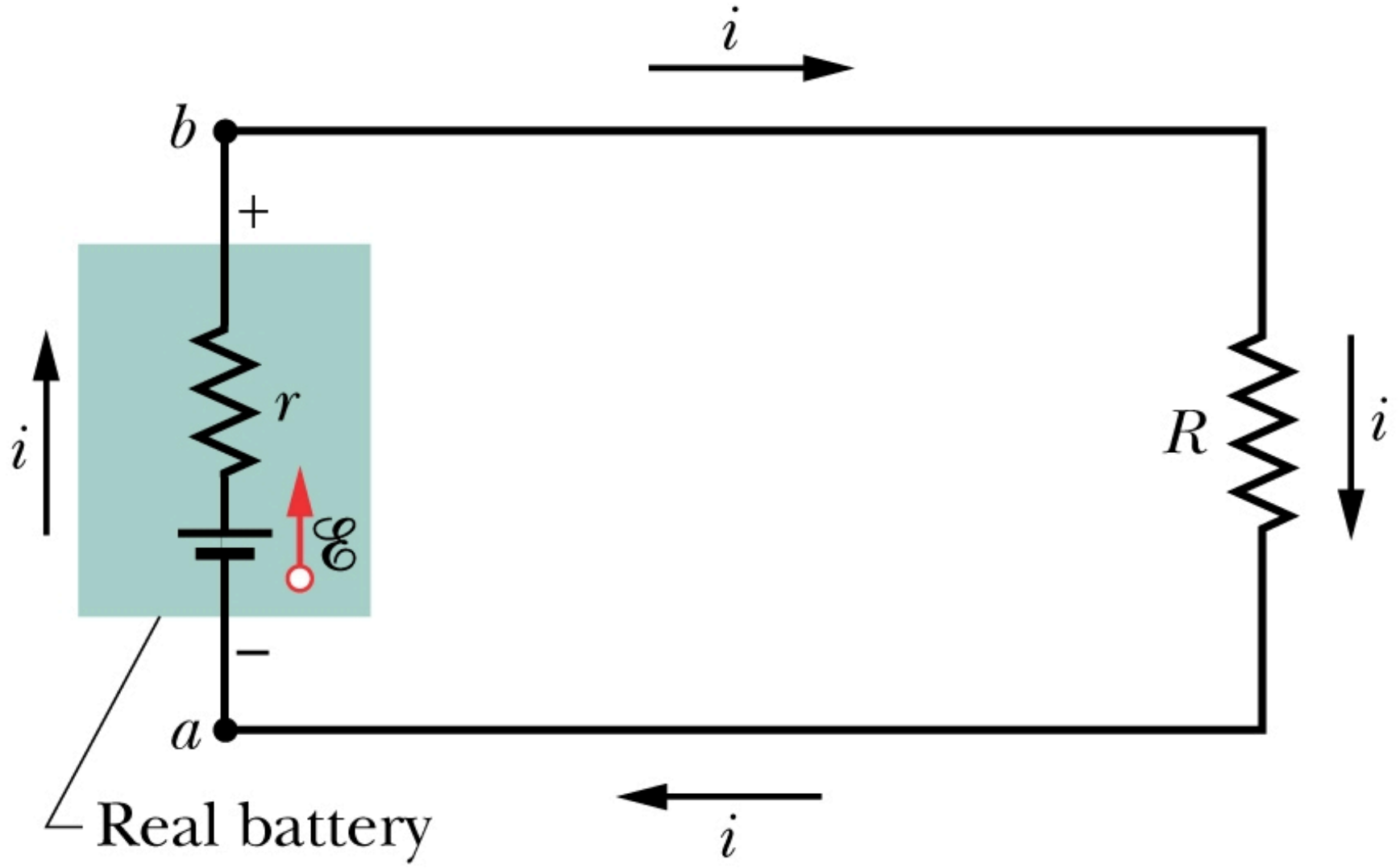

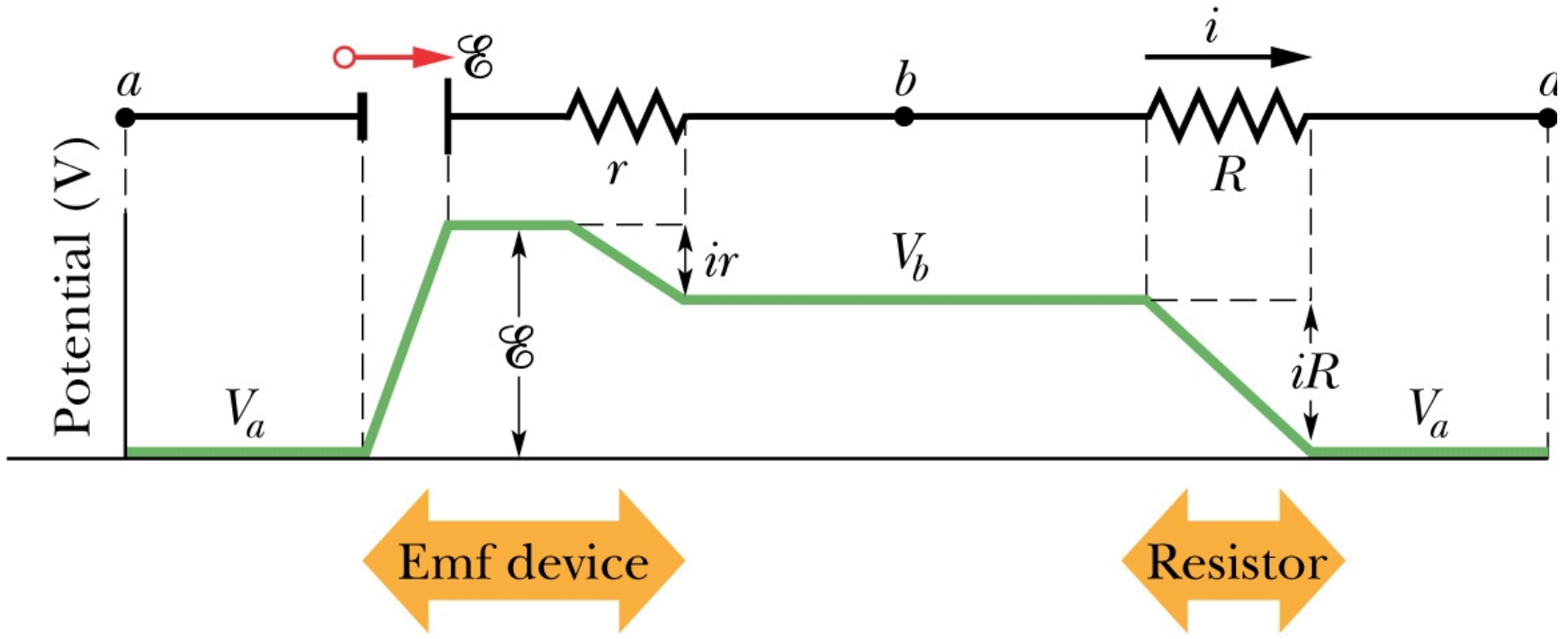

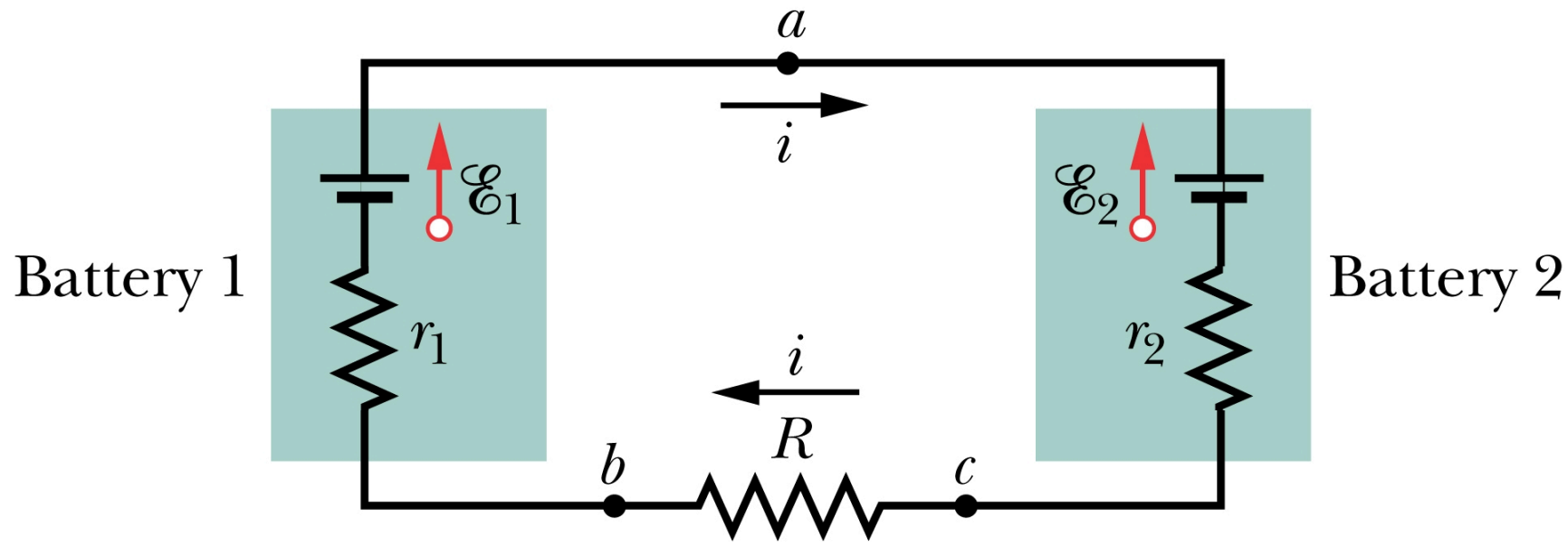

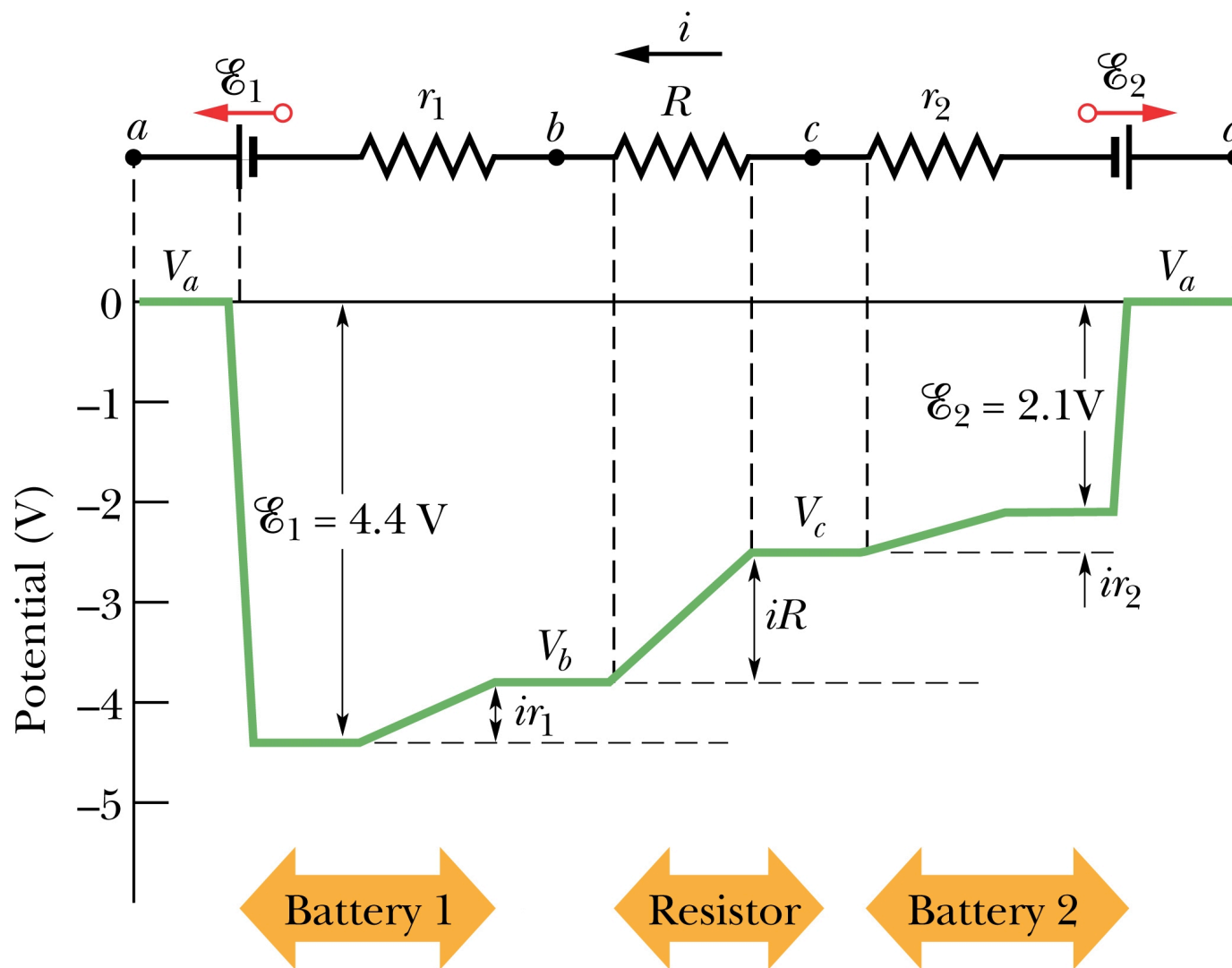

### Activity 23.11.1.

For many circuits, we don't know beforehand what the currents are in each branch, or even what direction they might be going in. In order to write Kirchhoff's equations, we have to pick a current direction, even if it isn't the direction the current is actually flowing in.

**Just pick a current direction for each branch, and move on.**

**Just pick a loop direction for each loop, and move on.**

- Part **a.** – In the example, they arbitrarily picked the current in the middle branch,  $i_2$ , to be flowing from top to bottom, and arbitrarily picked the 2 loop directions to be clockwise. Here, they want you to have the current in the middle branch flowing from bottom to top, and call it by a different name,  $i'_2$  (note the prime, it looks kind of funky in the figure.). They also want you to have the 2 loop directions be counterclockwise. (Hint: These changes will just change most (but not all) of the signs in equations 23.1, 23.2, and 23.3)
- Part **b.** – Take the 3 equations you came up with in Part **a.** and replace  $i'_2$  with  $-i_2$  in each one. Now rearrange them until they look like equations 23.1, 23.2, and 23.3.

# **WolframAlpha** computational knowledge engine.

Enter what you want to calculate or know about:

$68x + 100y + 0z = 4.5, 0x + 100y - 39z = 1.5, 1x - 1y - 1z = 0$



[Web Apps](#) [Examples](#) [Random](#)

Explore some of the things Wolfram|Alpha can do:

 <b>Mathematics</b>	 <b>Step-by-step Solutions</b>	 <b>Words &amp; Linguistics</b>	 <b>Units &amp; Measures</b>	 <b>Statistical &amp; Data Analysis</b>
 <b>People &amp; History</b>	 <b>Dates &amp; Times</b>	 <b>Chemistry</b>	 <b>Culture &amp; Media</b>	 <b>Money &amp; Finance</b>
 <b>Physics</b>	 <b>Art &amp; Design</b>	 <b>Socioeconomic Data</b>	 <b>Astronomy</b>	 <b>Music</b>
 <b>Health &amp; Medicine</b>	 <b>Engineering</b>	 <b>Places &amp; Geography</b>	 <b>Food &amp; Nutrition</b>	 <b>Education</b>
 <b>Materials</b>	 <b>Earth Sciences</b>	 <b>Life Sciences</b>	 <b>Weather &amp; Meteorology</b>	 <b>Technological World</b>
 <b>Sports &amp; Games</b>	 <b>Computational Sciences</b>	 <b>Transportation</b>	 <b>Web &amp; Computer Systems</b>	 <b>Surprises</b>

68x + 100y + 0z = 4.5, 0x + 100y - 39z = 1.5, 1x - 1y - 1z = 0



 Web Apps  Examples  Random

**Input:**

{68 x + 100 y + 0 z = 4.5, 0 x + 100 y - 39 z = 1.5, 1 x - 1 y - 1 z = 0}

Open code 

**Result:**

{68 x + 100 y = 4.5, 100 y - 39 z = 1.5, x - y - z = 0}

**Solution:**

$x \approx 0.0356126$ ,  $y \approx 0.0207834$ ,  $z \approx 0.0148292$

Step-by-step solution

Try it! 



**Alternate forms:**

$\{x + 1.47059 y = 0.0661765, y = 0.39 z + 0.015, x = y + z\}$



$\{y = 0.045 - \frac{17x}{25}, z = \frac{100y}{39} - 0.0384615, z = x - y\}$

$\{4(17x + 25y) = 4.5, 100y - 39z = 1.5, x - y - z = 0\}$



**Alternate form assuming x, y, and z are positive:**

$\{x + 1.47059 y = 0.0661765, y = 0.39 z + 0.015, x = y + z\}$

