

Unit 23.1 – 23.5

In Unit 22 → lots of observations

→ some measurements

⇒ Developed concepts, knowledge

So far, we have used only small lightbulbs.

We could also have used toaster, hairdryer, computer, etc.

For all cases, we would like to know:

→ **potential difference**, ΔV , across each element (bulb, etc.)

→ **current**, I , through each element and battery

Next 2 class – develop ways to **calculate** ΔV and I .

Today's class – continue to **measure** ΔV and I :

- practice connecting circuits and making measurements with voltmeters and ammeters.
- continue reinforcing our knowledge.
 - ⇒ lots of **predictions**.

So, what do we know?

Charge: – a property of an object (electron, proton, ion)

Current: – amount of charge (not # of objects) passing a location each second. $I \equiv \frac{q}{\Delta t}$

Wires: – conductors
– equipotential surfaces
→ electric potential is same everywhere on a wire

Batteries: – source of constant potential difference, ΔV , regardless of
– circuit connected to it
– current through it

Bulbs: – provide resistance
– need a ΔV across a bulb to light it
→ need a ΔV across a bulb to cause a **current** through the bulb
(cause) (effect)
– two bulbs in series have more resistance than a single bulb
– two bulbs in parallel have less resistance than a single bulb